

EE23BTECH11047 - Deepakreddy P

32 A single-phase full-bridge diode rectifier feeds a resistive load of 50Ω from a 200 V , 50 Hz single phase AC supply. If the diodes are ideal, then the active power, in watts, drawn by the load is (round off to nearest integer).

(GATE EE 32)

Solution:

Table I
INPUT PARAMETERS

Symbol	Description	value
R	Load Resistance	50Ω
V_{rms}	RMS Voltage	200V
f	Frequency	50Hz

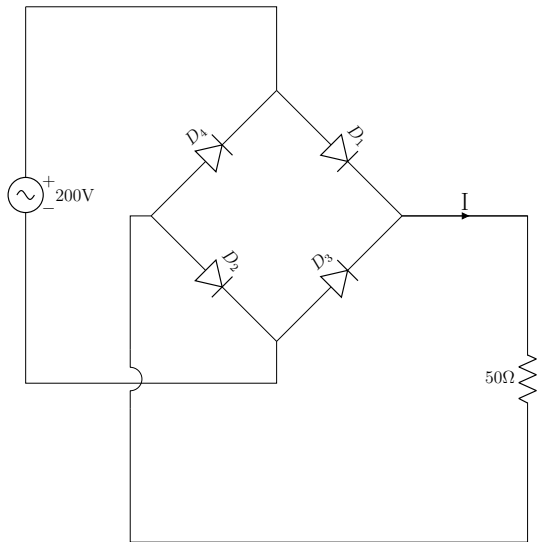


Figure 1. Circuit-1

$$V_{rms} = 200 \quad (1)$$

$$P = \frac{(V_{rms})^2}{R} \quad (2)$$

$$P = \frac{(200)^2}{50} W \quad (3)$$

$$P = 800W \quad (4)$$

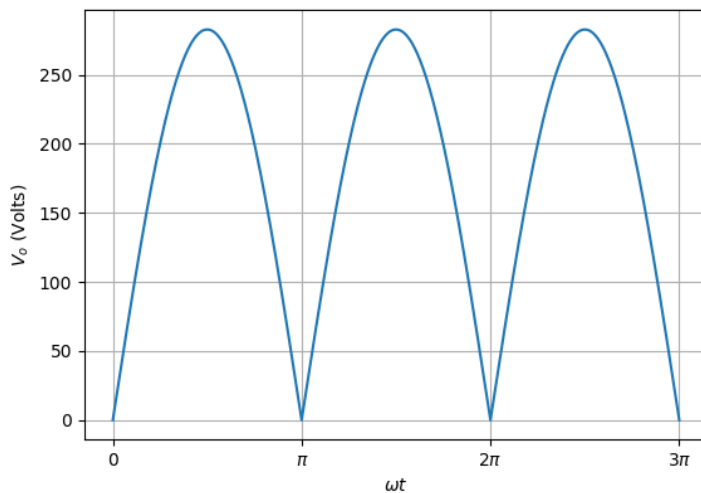


Figure 2. Output voltage waveform of single-phase full bridge rectifier